



哈爾濱工業大學 (深圳)
HARBIN INSTITUTE OF TECHNOLOGY

实验报告

开课学期: 2022 秋季

课程名称: 数字逻辑设计 (实验)

实验名称: 密码锁设计

实验性质: 综合设计型

实验学时: 6 地点: T2615

学生班级: 计科五班

学生学号: 210110504

学生姓名: 廖雨泰

评阅教师: _____

报告成绩: _____

实验与创新实践教育中心制

2022 年 12 月

设计的功能描述

概述基本功能、详细描述自行扩展的功能

基本功能：


- 1.按 S1 复位进入初始状态，数码管显示 00000000。
- 2.若已解锁，或未设置密码，按 S2 设置密码，通过 4*4 小键盘输入 3 位初始密码，输入的密码显示在显示屏上，且其余位不显示数字，输入满三位后按 S5 确定，成功后 GLD0 亮；
- 3.若已设置密码，按 S3 可以验证密码，通过小键盘逐位输入密码，输入的密码显示在显示屏上，且其余位不显示数字，输入满三位后按 S5 确定，如果正确则进入解锁状态，累计失败次数清零，不正确则累计失败次数+1，显示对应数量红灯，若累计 3 次则系统锁住，数码管显示 ffffffff，所有功能无效（除复位）。
- 4.每次进入新状态，数码管清除上个状态的输入。

系统功能详细设计

用硬件框图描述系统主要功能及各模块之间的相互关系

要求有信号名、位宽、模块说明，可以参考下面的框图（仅为示例），须有密码处理模块、

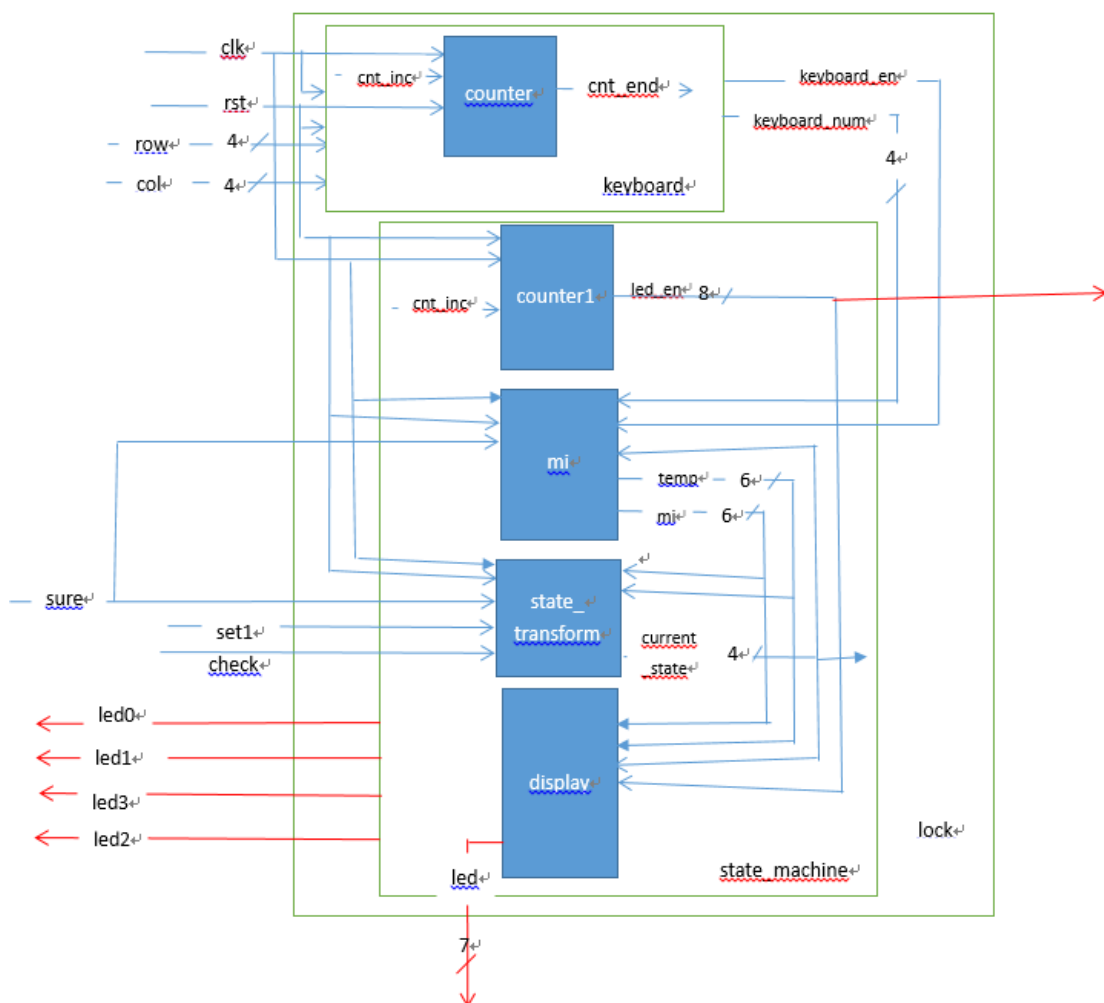数码管显示处理模块、按键处理模块，其他模块不限，不可用 vivado 的 RTL 截图。



模块说明：keyboard 为按键处理模块，其中的 counter 为计数器模块，

state_machine 为状态机模块，其中的 counter 为利用计数器制成的数码管使能信号发生模块，

mi 为处理密码和待验证的输入数字的密码处理模块，state_transform 为状态转换模块，display 为数码管显示处理模块

状态描述、状态转移图及状态编码，包括功能状态转移图、密码匹配的状态转移图；

状态描述：

IDLE：初始态，解锁状态，0000

s0：设置密码，0001

s1: 密码设置完成, 0010

s2: 校验密码, 0011

s3: 密码错误一次, 0100


s4: 校验密码, 0101

s5: 密码错误二次, 0110

s6: 校验密码, 0111

s7: 密码错误三次, 1000

功能状态转移图

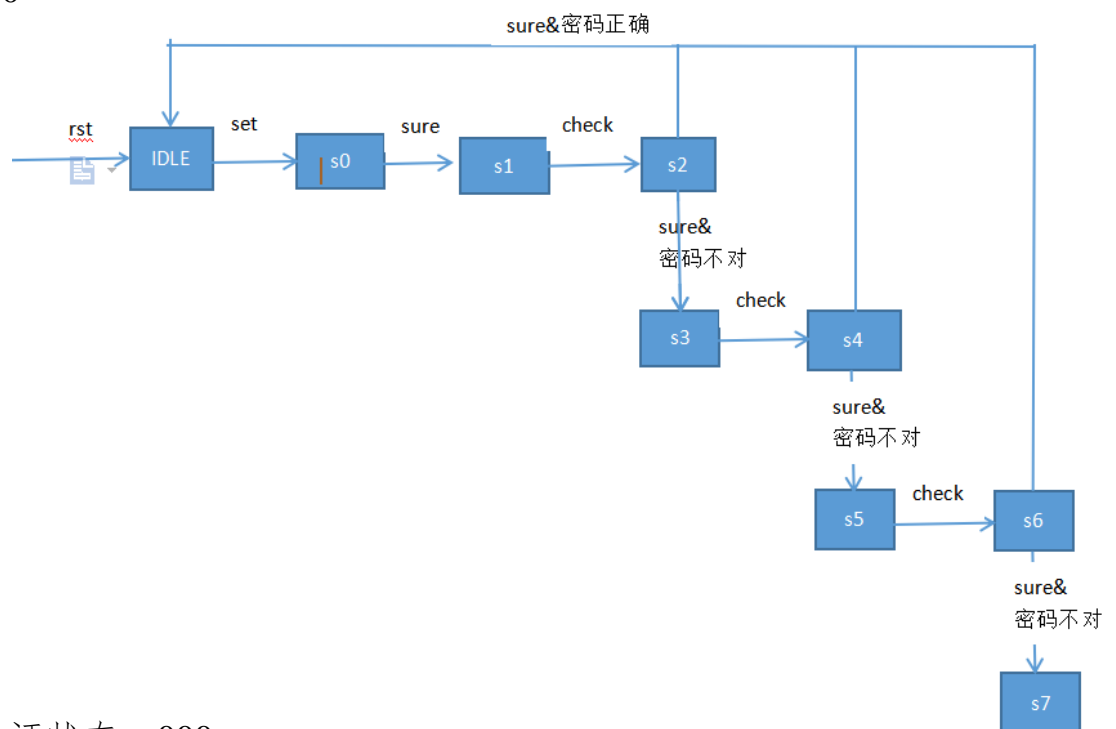

IDLE:初始态, 未开始验证状态, 000

A0:进入验证状态, 001


A1:匹配成功最高位, 010

A2:匹配成功第二位, 011

A3:匹配成功第三位, 100,

A4:匹配失败, 101

密码匹配状态转移图

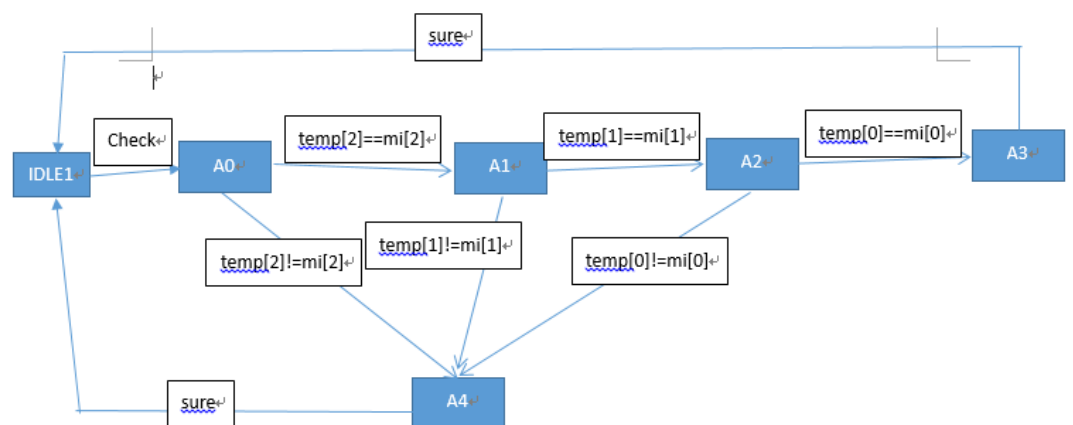

各模块描述

包括模块功能，输入、输出端口、变量含义及主要设计代码

硬件框图有的模块都需体现

counter:

功能：计数器

输入：clk（时钟信号）,rst（复位信号）,cnt_inc（计数使能信号）

输出：cnt_end（一轮计数结束信号）

主要设计代码：

```
always @(posedge clk, posedge reset) begin
```

```
    if (reset) cnt <= 0;
```

```
    else if (cnt_end) cnt <= 0;
```

```
    else if (cnt_inc) cnt <= cnt + 1;
```

```
end
```

keyboard:

功能：按键处理

输入：clk（时钟信号）,rst（复位信号）

row(读取行输入信号)

输出：col(输出列扫描信号)keyboard_en(按键值有效信号)

keyboard_num(按键值)

主要设计代码：

```
always @(posedge clk, posedge reset) begin
```

```
if (reset == 1) begin

    keyboard_num <= 0;

end else if (key_posedge) begin

    if (key_posedge[0]) keyboard_num <= 'hd;
    else if (key_posedge[1]) keyboard_num <= 'hc;
    else if (key_posedge[2]) keyboard_num <= 'hb;
    else if (key_posedge[3]) keyboard_num <= 'ha;
    else if (key_posedge[4]) keyboard_num <= 'hf;
    else if (key_posedge[5]) keyboard_num <= 'h9;
    else if (key_posedge[6]) keyboard_num <= 'h6;
    else if (key_posedge[7]) keyboard_num <= 'h3;
    else if (key_posedge[8]) keyboard_num <= 'h0;
    else if (key_posedge[9]) keyboard_num <= 'h8;
    else if (key_posedge[10]) keyboard_num <= 'h5;
    else if (key_posedge[11]) keyboard_num <= 'h2;
    else if (key_posedge[12]) keyboard_num <= 'he;
    else if (key_posedge[13]) keyboard_num <= 'h7;
    else if (key_posedge[14]) keyboard_num <= 'h4;
    else if (key_posedge[15]) keyboard_num <= 'h1;

end else begin

    keyboard_num <= 0;

end
```

```
end

always @(posedge clk, posedge reset) begin

    if (reset == 1) begin

        keyboard_en <= 0;

    end else if (key_posedge) begin

        keyboard_en <= 1;

    end else begin

        keyboard_en <= 0;

    end

end

always @(posedge clk, posedge reset) begin

    if (reset == 1)

        keyboard_led <= 0;

    else

        keyboard_led <= key;

    end

end

always @(posedge clk, posedge reset) begin

    if (reset == 1)          col <= 4'b1111;

    else if (col == 4'b1111) col <= 4'b1110;

    else if (cnt_end)        col <= {col[2:0], col[3]};
```

```
end
```

```
always @(posedge clk, posedge reset) begin
```

```
    if (reset == 1) key_r <= 0;
```

```
    else key_r <= key;
```

```
end
```

```
always @(posedge clk, posedge reset) begin
```

```
    if (reset == 1) key <= 0;
```

```
    else if (cnt_end) begin
```

```
        if (col[0] == 0) key[3:0]    <= ~row;
```

```
        if (col[1] == 0) key[7:4]    <= ~row;
```

```
        if (col[2] == 0) key[11:8]   <= ~row;
```

```
        if (col[3] == 0) key[15:12] <= ~row;
```

```
    end
```

```
end
```

counter1:

功能：产生数码管使能信号

输入：clk（时钟信号）,rst（复位信号）,cnt_inc（计数使能信号）

输出：led_en（数码管使能信号）

主要设计代码：

counter 源代码+

```
always @(posedge clk or posedge rst)
```

```
begin
```

```
if(rst) led_en <= 8'b11111110;
```

```
else if(cnt_end) led_en<={led_en[6:0],led_en[7]};
```

```
end
```

mi 模块:

功能：读入设定密码和验证密码

输入：rst（复位信号）,sure(确认信号),keyboard_num（按键值），clk（时钟信号）

keyboard_en（按键值有效信号）,current_state（当前状态）

输出：temp（待验证密码），mi(设定密码)

主要设计代码：

```
always @(posedge clk or posedge rst)
```

```
//计数
```

```
begin
```

```
if(rst) n<=2'b10;
```

```
else if(sure)n<=2'b10;
```

```
else
```

```
if(((current_state==s2)|(current_state==s6)|(current_state==s4)|(current_state==s0))&keyboard_en)
```

```
n<=n-2'b01;
```

```
end
```

```
always @(posedge clk or posedge rst)
begin
if(rst) temp<=6'd0;
else if((current_state==s2)|(current_state==s6)|(current_state==s4))
    begin
        if((n==2'b10)&keyboard_en)
            begin
                case(keyboard_num)
                    4'd1:temp[5:4]<=2'b01;
                    4'd2:temp[5:4]<=2'b10;
                    4'd3:temp[5:4]<=2'b11;
                    default:temp[5:4]<=2'b00;
                endcase
            end
        else if((n==2'b01)&keyboard_en)
            begin
                case(keyboard_num)
                    4'd1:temp[3:2]<=2'b01;
                    4'd2:temp[3:2]<=2'b10;
                    4'd3:temp[3:2]<=2'b11;
                    default:temp[3:2]<=2'b00;
                endcase
            end
        end
    end
```

```
end

else if((n==2'b00)&keyboard_en)

begin

case(keyboard_num)

4'd1:temp[1:0]<=2'b01;

4'd2:temp[1:0]<=2'b10;

4'd3:temp[1:0]<=2'b11;

default:temp[1:0]<=2'b00;

endcase

end

end

else if(!((current_state==s2)|(current_state==s6)|(current_state==s4))) temp<=6'd0;

end

always @(posedge clk or posedge rst)

begin

if(rst) mi<=6'd0;

else if(current_state==s0)

begin

if((n==2'b10)&keyboard_en)

begin

case(keyboard_num)
```

```
4'd1:mi[5:4]<=2'b01;

4'd2:mi[5:4]<=2'b10;

4'd3:mi[5:4]<=2'b11;

default:mi[5:4]<=2'b00;

endcase

end

else if((n==2'b01)&keyboard_en)

begin

case(keyboard_num)

4'd1:mi[3:2]<=2'b01;

4'd2:mi[3:2]<=2'b10;

4'd3:mi[3:2]<=2'b11;

default:mi[3:2]<=2'b00;

endcase

end

else if((n==2'b00)&keyboard_en)

begin

case(keyboard_num)

4'd1:mi[1:0]<=2'b01;

4'd2:mi[1:0]<=2'b10;

4'd3:mi[1:0]<=2'b11;

default:mi[1:0]<=2'b00;
```

```
endcase
```

```
end
```

```
end
```

```
else if(current_state==IDLE)mi<=6'd0;
```

```
end
```

state_transform 模块:

功能: 状态转换

输入: mi(设定密码), temp (验证密码), rst (复位信号), clk(时钟信号)

sure (确认按键), set (设置密码信号), check (检验密码信号)

输出: current_state(当前状态)

主要设计代码:

```
always @(posedge clk or posedge rst)
```

```
begin
```

```
if(rst) current_state<=IDLE;
```

```
else current_state<=next_state;
```

```
end
```

```
always @(*)
```

```
begin
```

```
case(current_state)
```

```
    IDLE:if(set) next_state=s0;
```

```
        else next_state=IDLE;

s0:if(sure) next_state=s1;

        else next_state=s0;

s1:if(check)next_state=s2;

        else next_state=s1;

s2:if(sure&(temp==mi)) next_state=IDLE;

        else if(sure) next_state=s3;

        else next_state=s2;

s3:if(check)next_state=s4;

        else next_state=s3;

s4:if(sure&(temp==mi)) next_state=IDLE;

        else if(sure) next_state=s5;

        else next_state=s4;

s5:if(check)next_state=s6;

        else next_state=s5;

s6:if(sure&(temp==mi)) next_state=IDLE;

        else if(sure) next_state=s7;

        else next_state=s6;

default:next_state=s7;

endcase

end
```

display 模块:

功能: 产生数码管显示信号

输入: led_en (数码管使能信号), current_state (当前状态), mi(密码),

temp (待验证密码)

输出: led (数码管显示信号)

主要设计代码:

```
always@(*)
```

```
begin
```

```
case(current_state)
```

```
    IDLE:led=7'b00000001;
```

```
    s0:case(led_en)
```

```
        8'b11011111:case(mi[1:0])
```

```
            2'b01:led=7'b10011111;
```

```
            2'b10:led=7'b0010010;
```

```
            2'b11:led=7'b0000110;
```

```
            default:led=7'b1111111;
```

```
        endcase
```

```
    8'b10111111:case(mi[3:2])
```

```
        2'b01:led=7'b10011111;
```

```
        2'b10:led=7'b0010010;
```

```
        2'b11:led=7'b0000110;
```

```
        default:led=7'b1111111;
```

```
endcase
```

```
8'b01111111:case(mi[5:4])
```

```
2'b01:led=7'b1001111;
```

```
2'b10:led=7'b0010010;
```

```
2'b11:led=7'b0000110;
```

```
default:led=7'b1111111;
```

```
endcase
```

```
default:led=7'b1111111;
```

```
endcase
```

```
s1:led=7'b1111111;
```

```
s5:led=7'b1111111;
```

```
s3:led=7'b1111111;
```

```
s7:led=7'b0111000;
```

```
default:case(led_en)
```

```
8'b11011111:case(temp[1:0])
```

```
2'b01:led=7'b1001111;
```

```
2'b10:led=7'b0010010;
```

```
2'b11:led=7'b0000110;
```

```
default:led=7'b1111111;
```

```
endcase
```

```
8'b10111111:case(temp[3:2])
```

```
2'b01:led=7'b1001111;
```



```
        2'b10:led=7'b0010010;

        2'b11:led=7'b0000110;

        default:led=7'b1111111;

    endcase

    8'b01111111:case(temp[5:4])

        2'b01:led=7'b1001111;

        2'b10:led=7'b0010010;

        2'b11:led=7'b0000110;

        default:led=7'b1111111;

    endcase

    default:led=7'b1111111;



endcase
```

```
endcase
```

```
end
```

调试报告

仿真波形截图及仿真分析

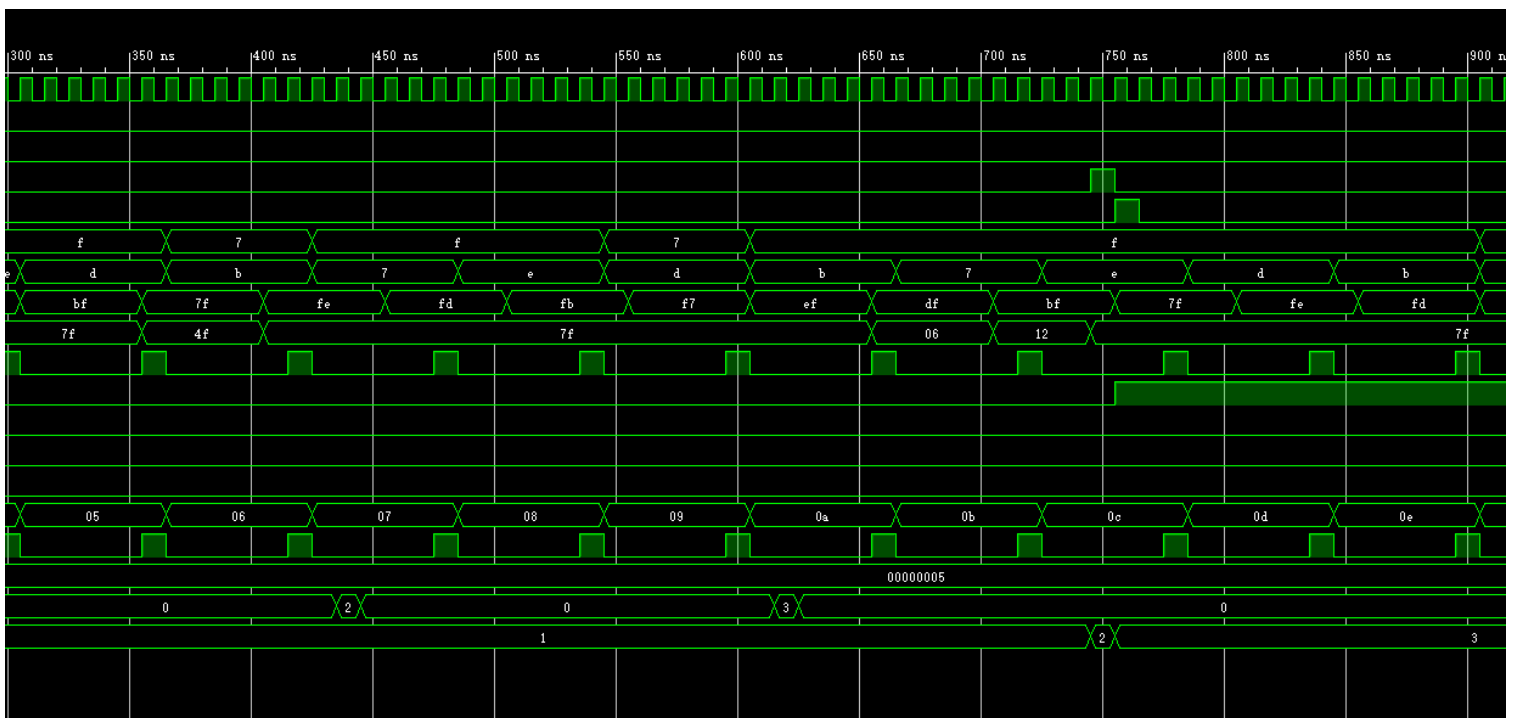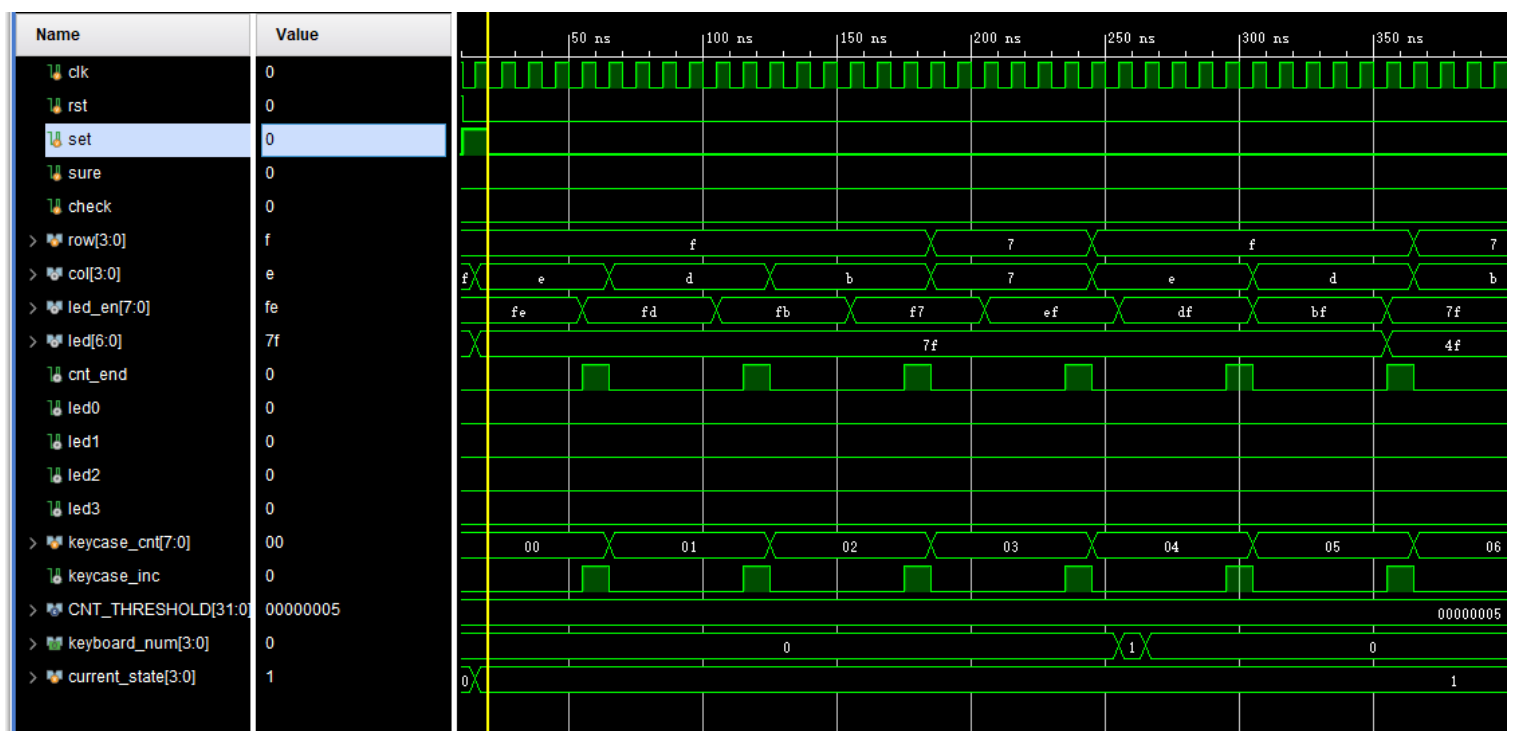

密码设定:


初始态: clk 为 0, rst 为 1, sure 为 0, set 为 0, check 为 0, current_state 为 0, 符合预期

10ns 时, set 变为 1, current_state 变为 1, 符合预期。

后续直到 725ns, row 和 col 不断变化, 设定密码输入, 745ns 时, sure 变为 1, current_state 变为 2, led0 变为 1, 符合预期


密码匹配:

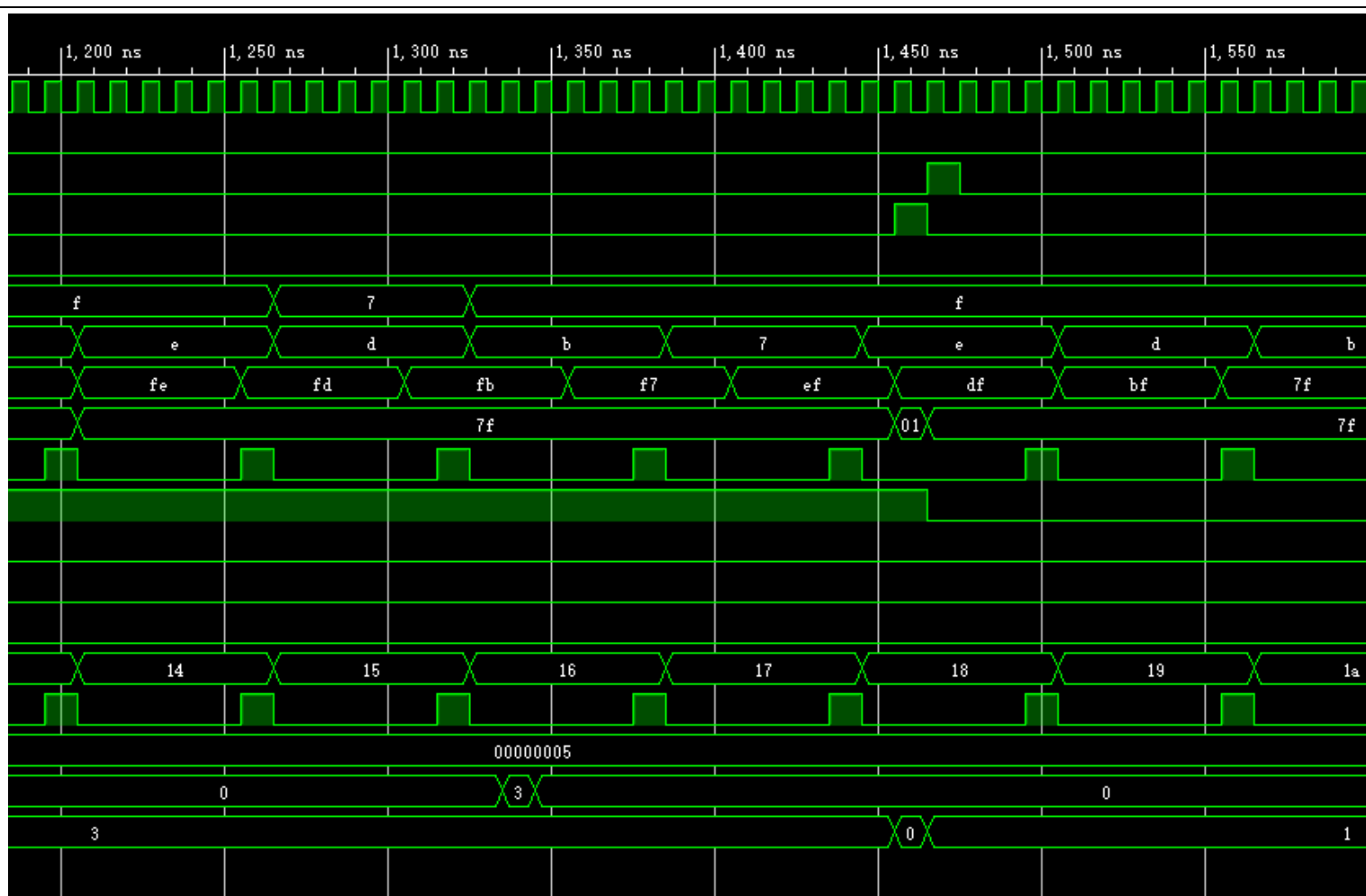775ns 时, check 变为 1, current_state 变为 3, 符合预期



密码匹配成功:

 
后续直到 1445ns,row 和 col 不断变化, 检验密码输入, 1455ns 时, sure 变为 1, 解锁成功, current_state 变为 0, led0 也变为 0, 符合预期



密码匹配失败:

2800ns 时, current_state 为 3。

 2905ns 时, sure=1, 密码错误, current_state 变为 4, led1 变为 1, 符合预期



密码锁定:

4250ns 时, current_state 为 7。

4345ns 时, sure 为 1, 密码错误, current_state 变为 8, led3 变为 1, 锁定, 符合预期。

设计过程中遇到的问题及解决方法

1. 按键与 `keyboard_led` 对应不上，一个一个试验后对应好
2. 按键输入时一个数字会输入很多次，将 `keyboard_led` 改为用 `keyboard_en` 和 `keyboard_num`
3. `led1`, `led2`, `led3` 进入另一状态时自动熄灭，改组合逻辑为时序逻辑
4. 密码匹配未用状态机实现，重新写密码匹配

课程设计总结

包括设计的总结和还需改进的内容以及收获

总结：

- 1.时序逻辑和组合逻辑要分清什么时候用哪个
- 2.只有两个信号能以边沿触发的形式出现在敏感信号列表里

需要改进的内容：

对我来说工程量较大，后续几次作业几乎每次都要课下来机房 2-4 次，除了一次作业外，其他作业都对我有较大提升，所以我认为可以删掉中间一次较为简单的项目，将时间分配给其他几次作业，这样并不会影响学生的阶梯型提升

收获：

verilog 代码能力上升，对组合逻辑和时序逻辑有了更深的理解，代码更加规范。

